

Binary to BCD Converter

Shift and Add-3 Algorithm

1. Shift the binary number left one bit.
2. If 8 shifts have taken place, the BCD number is in the *Hundreds*, *Tens*, and *Units* column.
3. If the binary value in any of the BCD columns is 5 or greater, add 3 to that value in that BCD column.
4. Go to 1.

Operation	Hundreds	Tens	Units	Binary	
HEX				F	F
Start				1 1 1 1	1 1 1 1


Example 1: Convert hex **E** to BCD

Operation	Tens	Units	Binary
HEX			E
Start			1 1 1 0
Shift 1		1	1 1 0
Shift 2		1 1	1 0
Shift 3		1 1 1	0
Add 3		1 0 1 0	0
Shift 4	1	0 1 0 0	
BCD	1	4	

Example 2: Convert hex **FF** to BCD

Operation	Hundreds	Tens	Units	Binary	
HEX				F	F
Start				1 1 1 1	1 1 1 1
Shift 1			1	1 1 1 1	1 1 1
Shift 2			1 1	1 1 1 1	1 1
Shift 3			1 1 1	1 1 1 1	1
Add 3			1 0 1 0	1 1 1 1	1
Shift 4		1	0 1 0 1	1 1 1 1	
Add 3		1	1 0 0 0	1 1 1 1	
Shift 5		1 1	0 0 0 1	1 1 1	
Shift 6		1 1 0	0 0 1 1	1 1	
Add 3		1 0 0 1	0 0 1 1	1 1	
Shift 7	1	0 0 1 0	0 1 1 1	1	
Add 3	1	0 0 1 0	1 0 1 0	1	
Shift 8	1 0	0 1 0 1	0 1 0 1		
BCD	2	5	5		

Truth table for Add-3 Module

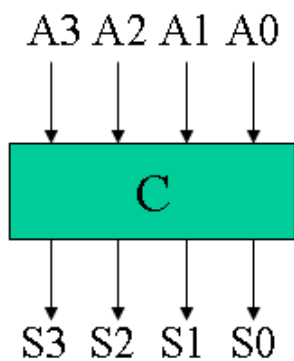

A3	A2	A1	A0	S3	S2	S1	S0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	1	0	0
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Here is a Verilog module for this truth table.

```

module add3(in,out);
input [3:0] in;
output [3:0] out;
reg [3:0] out;


```

```

always @ (in)
  case (in)
    4'b0000: out <= 4'b0000;
    4'b0001: out <= 4'b0001;
    4'b0010: out <= 4'b0010;
    4'b0011: out <= 4'b0011;
    4'b0100: out <= 4'b0100;
    4'b0101: out <= 4'b1000;
    4'b0110: out <= 4'b1001;
    4'b0111: out <= 4'b1010;
    4'b1000: out <= 4'b1011;
    4'b1001: out <= 4'b1100;
    default: out <= 4'b0000;
  endcase
endmodule

```

Binary-to-BCD Converter Module

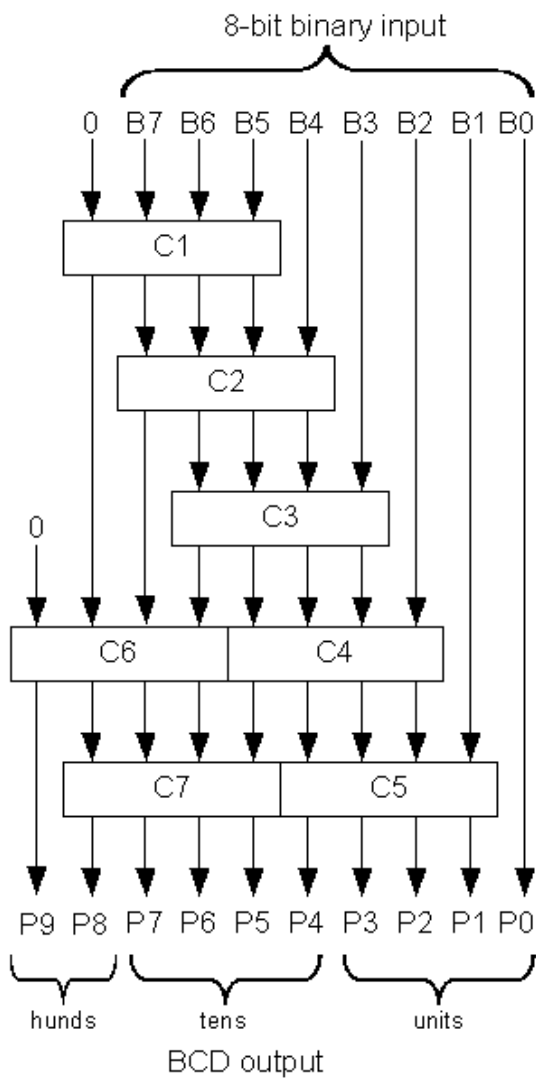

Here is a structural Verilog module corresponding to the logic diagram.

```

module binary_to_BCD(A,ONES,TENS,HUNDREDS);
input [7:0] A;
output [3:0] ONES, TENS;
output [1:0] HUNDREDS;
wire [3:0] c1,c2,c3,c4,c5,c6,c7;
wire [3:0] d1,d2,d3,d4,d5,d6,d7;

assign d1 = {1'b0,A[7:5]};
assign d2 = {c1[2:0],A[4]};
assign d3 = {c2[2:0],A[3]};

```

```
assign d4 = {c3[2:0],A[2]};
assign d5 = {c4[2:0],A[1]};
assign d6 = {1'b0,c1[3],c2[3],c3[3]};
assign d7 = {c6[2:0],c4[3]};
add3 m1(d1,c1);
add3 m2(d2,c2);
add3 m3(d3,c3);
add3 m4(d4,c4);
add3 m5(d5,c5);
add3 m6(d6,c6);
add3 m7(d7,c7);
assign ONES = {c5[2:0],A[0]};
assign TENS = {c7[2:0],c5[3]};
assign HUNDREDS = {c6[3],c7[3]};

endmodule
```

General Binary-to-BCD Converter

The linked code is a general [binary-to-BCD](#) Verilog module, but I have not personally tested the code.

Reference: course materials from [Prof. Richard E. Haskell](#)

Maintained by [John Loomis](#), last updated *4 Jan 2004*