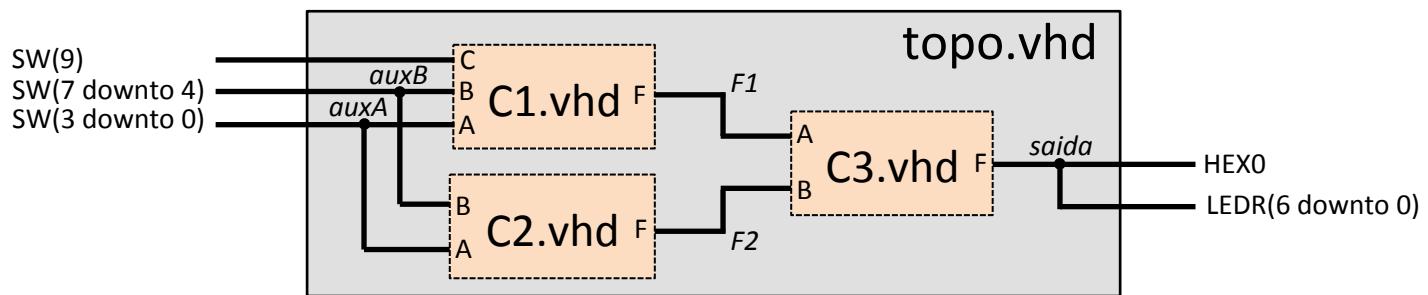


-- UFSC - EEL 5105 - Circuitos e Tecnicas Digitais
-- Prof. Eduardo Augusto Bezerra <Eduardo.Bezerra@ufsc.br>
-- Exemplo de uso de componentes em VHDL. Data da ultima alteracao: 11 de setembro de 2019.
-- Arquivos componentes desse projeto: topo.vhd, C1.vhd, C2.vhd e C3.vhd



```
-- topo.vhd
library ieee;
use ieee.std_logic_1164.all;

entity topo is
    port ( SW: in std_logic_vector(9 downto 0);
           LEDR: out std_logic_vector(9 downto 0);
           HEX0: out std_logic_vector(6 downto 0)
        );
end topo;

architecture topo_bhv of topo is

    signal auxA,auxB: std_logic_vector(3 downto 0);
    signal F1,F2: std_logic_vector(3 downto 0);
    signal saida: std_logic_vector(6 downto 0);

    component C1
        port ( A: in std_logic_vector(3 downto 0);
               B: in std_logic_vector(3 downto 0);
               C: in std_logic;
               F: out std_logic_vector(3 downto 0)
            );
    end component;
    component C2
        port ( A: in std_logic_vector(3 downto 0);
               B: in std_logic_vector(3 downto 0);
               F: out std_logic_vector(3 downto 0)
            );
    end component;
    component C3
        port ( A: in std_logic_vector(3 downto 0);
               B: in std_logic_vector(3 downto 0);
               F: out std_logic_vector(6 downto 0)
            );
    end component;

begin      -- BEGIN da architecture

    auxA <= SW(3 downto 0);
    auxB <= SW(7 downto 4);

    U1: C1 port map (auxA, auxB, SW(9), F1);
    U2: C2 port map (auxA, auxB, F2);
    U3: C3 port map (F1, F2, saida);

    LEDR(6 downto 0) <= saida;
    HEX0 <= saida;

end topo_bhv;      -- END da architecture
```

```
-- C1.vhd (expressoes logicas e mux)
library IEEE;
use IEEE.Std_Logic_1164.all;

entity C1 is
    port ( A: in std_logic_vector(3 downto 0);
           B: in std_logic_vector(3 downto 0);
           C: in std_logic;
           F: out std_logic_vector(3 downto 0)
        );
end C1;
architecture c1_bhv of C1 is
begin
    F <= (A or B) when C = '1' else
                  (A and B);
end c1_bhv;
```

```
-- C2.vhd  (expressao logica)
library IEEE;
use IEEE.Std_Logic_1164.all;

entity C2 is
    port ( A: in std_logic_vector(3 downto 0);
           B: in std_logic_vector(3 downto 0);
           F: out std_logic_vector(3 downto 0)
        );
end C2;
architecture c2_bhv of C2 is
begin
    F <= A xor B;
end c2_bhv;
```

```
-- C3.vhd  (decodificador)
library IEEE;
use IEEE.Std_Logic_1164.all;

entity C3 is
    port ( A: in std_logic_vector(3 downto 0);
           B: in std_logic_vector(3 downto 0);
           F: out std_logic_vector(6 downto 0)
        );
end C3;
architecture c3_bhv of C3 is
begin
    F <= "1001000" when A = "0000" else
                  "0000011" when B = "0000" else
                  "0000110";
end c3_bhv;
```